

💡 姓名：葉致廷/林廷濤
學號：0846013/0846011




- **Description**

- **Different type instruction construction_Fig1**

Lab 3: Single-Cycle CPU (Simple Version)

 - **SB type immediate value construction_Fig2**



- **Source Code**

```
module Imm_Gen(input [31:0] instr_i,
               output [31:0] Imm_Gen_o);

    /* Write your code HERE */
    reg [31:0] Imm_Gen_out;
    wire [7:1:0] opcode = instr_i[6:0];

    always@ *
    begin
        case(opcode)
            // R_type
            7'b0110011: Imm_Gen_out <= instr_i;
            // Load
            7'b0000011:
            begin
                Imm_Gen_out <= {{20{instr_i[31]}}, instr_i[31:20]};
            end
            // STORE
            7'b0100011:
            begin
                Imm_Gen_out <= {{20{instr_i[31]}}, instr_i[31:25], instr_i[11:7]};
            end
            // I_type Imm
            7'b0010011:
            begin
                Imm_Gen_out <= {{20{instr_i[31]}}, instr_i[31:20]};
            end
            // SB
            7'b1100011:
            begin
                Imm_Gen_out <= {{20{instr_i[31]}}, instr_i[31], instr_i[7], instr_i[30:25], instr_i[11:8]};
            end
        endcase
    end

    assign Imm_Gen_o = Imm_Gen_out;

endmodule
```

- **Shift_Left_1 Module**

- **Description**

此Module功能單純，就是把input(也就是Immediate value)左移一位即可，操作上取32bit input的[30:0]，然後LSB補0即可：`assign data_o = {data_i[30:0], 1'b0};`

- **Source Code**

```
module Shift_Left_1(input [32-1:0] data_i,
                   output [32-1:0] data_o);
```

```

/* Write your code HERE */
assign data_o = {data_i[30:0], 1'b0};

endmodule

```

• **ALU_Ctrl Module**

• **Description**

此Module主要是透過輸入的ALUOp，與Instruction3/4個bit，來輸出我們自定義的ALU Control Input。相關定義如下：



ALUOp Type

00: Load/Store/Immediate

01: SB Type

10: R Type



Different Action depend on instruction, customized define the ALU Control Input

ALUOp Type: 0 ⇒ depend on first 3 bit of instruction

000 ⇒ ADDI ⇒ output: 2

010 ⇒ SLTI ⇒ output: 7

100 ⇒ XORI ⇒ output: 13

110 ⇒ ORI ⇒ output: 1

111 ⇒ ANDI ⇒ output: 0

001 ⇒ SLLI ⇒ output: 3

101 ⇒ SRLI ⇒ output: 5

ALUOp Type: 1 ⇒ depend on first 3 bit of instruction

000 ⇒ BEQ ⇒ output: 10

001 ⇒ BNE ⇒ output: 11

ALUOp Type: 2 ⇒ depend on first 4 bit of instruction

0111 ⇒ AND ⇒ output: 0

0110 ⇒ OR ⇒ output: 1

0000 ⇒ ADD ⇒ output: 2

0001 ⇒ SLL ⇒ output: 3

0101 ⇒ SRL ⇒ output: 4

0010 ⇒ SLT ⇒ output: 7

0100 ⇒ XOR ⇒ output: 13

1000 ⇒ SUB ⇒ output: 6

1101 ⇒ SRA ⇒ output: 5

• **Source Code**

```

module ALU_Ctrl(input [4-1:0] instr,
                input [2-1:0] ALUOp,
                output [4-1:0] ALU_Ctrl_o);

```

```

/* Write your code HERE */
reg [4-1:0] ALU_Ctrl_out;

always@*
begin
case(ALUOp)
/* Load, Store, Imm*/
2'b00:
begin
case(instr[3-1:0])
//ADDI do add
3'b000: ALU_Ctrl_out <= 4'b0010;
//SLTI do slt
3'b010: ALU_Ctrl_out <= 4'b0111;
//XORI do xor:13
3'b100: ALU_Ctrl_out <= 4'b1101;
//ORI do or
3'b110: ALU_Ctrl_out <= 4'b0001;
//ANDI do and
3'b111: ALU_Ctrl_out <= 4'b0000;
//SLLI do sll:3
3'b001: ALU_Ctrl_out <= 4'b0011;
//SRAI do sra:5
3'b101: ALU_Ctrl_out <= 4'b0101;
endcase
end
/* SB */
2'b01:
begin
case(instr[3-1:0])
//BEQ do beq:10
3'b000: ALU_Ctrl_out <= 4'b1010;
//BNE do bne:11
3'b001: ALU_Ctrl_out <= 4'b1011;
endcase
end
/* R */
2'b10:
begin
case(instr)
//AND do and: 0
4'b0111: ALU_Ctrl_out <= 4'b0000;
//OR do or: 1
4'b0110: ALU_Ctrl_out <= 4'b0001;
//ADD do add: 2
4'b0000: ALU_Ctrl_out <= 4'b0010;
//SLL do sll: 3
4'b0001: ALU_Ctrl_out <= 4'b0011;
//SRL do srl: 4
4'b0101: ALU_Ctrl_out <= 4'b0100;
//SLT do slt: 7
4'b0010: ALU_Ctrl_out <= 4'b0111;
//XOR do xor :13
4'b0100: ALU_Ctrl_out <= 4'b1101;
//SUB do sub: 6
4'b1000: ALU_Ctrl_out <= 4'b0110;
//SRA do sra: 5
4'b1101: ALU_Ctrl_out <= 4'b0101;
//NOR: 12

endcase
end
endcase
end

assign ALU_Ctrl_o = ALU_Ctrl_out;
endmodule

```

- **alu Module**

- **Description**

根據ALU_Ctrl Module所自定義的ALU Control Input, alu Module就要針對這些Control Input做不同的操作。舉例來說, 當 `ALU_control = 12`, 操作動作為 `NOR`, 輸出就為: `result <= ~(src1 | src2);`

- **Source Code**

```
module alu(input rst_n,
          input  [32-1:0] src1,
          input  [32-1:0] src2,
          input  [4-1:0] ALU_control,
          output reg [32-1:0] result,
          output reg zero,
          output reg cout,
          output reg overflow);

/* Write your code HERE */
wire [32-1:0] result_wire;
wire          carryout;
wire          overflow_wire;
wire          zeroWire;
assign zeroWire = (result == 0) ? 1'b1 :1'b0 ;

always @*
begin
if (rst_n) begin
    cout    <= 1'b0; //Don't care
    overflow <= 1'b0; //Don't care

    case(ALU_control)
        /* AND :0*/
        4'b0000:
        begin
            result = src1 & src2;
            zero = zeroWire;
        end
        /* OR :1*/
        4'b0001:
        begin
            result = src1 | src2;
            zero = zeroWire;
        end
        /* ADD :2*/
        4'b0010:
        begin
            result = src1 + src2;
            zero = zeroWire;
        end
        /* SUB :6*/
        4'b0110:
        begin
            result = src1 - src2;
            zero = zeroWire;
        end
        /* SLT :7*/
        4'b0111:
        begin
            result = (src1 < src2)?1:0;
            zero = zeroWire;
        end
        /* NOR :12*/
        4'b1100:
        begin
            result = ~(src1 | src2);
            zero = zeroWire;
        end
        /* XOR :13*/
        4'b1101:
        begin
            result = src1 ^ src2;
            zero = zeroWire;
        end
    endcase
end
end
```

```

        end
        /* SLL :3*/
        4'b0011:
        begin
            result = src1 << src2;
            zero = zeroWire;
        end
        /* SRL :4*/
        4'b0100:
        begin
            result = src1 >> src2;
            zero = zeroWire;
        end
        /* SRA :5*/
        4'b0101:
        begin
            result = src1 >>> src2;
            zero = zeroWire;
        end
        /* BEQ :10*/
        4'b1010:
        begin
            result = src1 - src2;
            zero = zeroWire;
        end
        /* BNE :11*/
        4'b1011:
        begin
            result = (src1 ^ src2) != 32'b0 ? 32'd0: 32'd1;
            zero = zeroWire;
        end

        default: result = 32'd0;

    endcase
end
end
endmodule

```

- **Adder Module**

- **Description**

此Module會用在Adder1(Program Counter+4)和Adder2(Program Counter+shift immediate value)中。此模組功能單純，就是把兩輸入相加在輸出而已。

- **Source Code**

```

module Adder(input [32-1:0] src1_i,
             input [32-1:0] src2_i,
             output [32-1:0] sum_o);

    /* Write your code HERE */
    assign sum_o = src1_i + src2_i;

endmodule

```

- **MUX_2to1 Module**

- **Description**

此Module會用在Mux_ALUSrc(由ALUSrc輸入來決定要輸出Read data2或是Immediate value)和Mux_PC Src(由PC Src輸入來決定要輸出PC+4還是PC+OFFSET)中。此模組功能單純，根據select_i輸入來決定要輸出data0_i或是data1_i。

- **Source Code**

```

module MUX_2to1(input [32-1:0] data0_i,
               input [32-1:0] data1_i,
               input  select_i,
               output [32-1:0] data_o);

  reg [32-1:0] data_out;
  /* Write your code HERE */
  always@(*)begin
    if (!select_i) begin//sel = 0 output_Z = input_A
      data_out = data0_i;
    end
    else begin//sel = 1 output_Z = input_B
      data_out = data1_i;
    end
  end

  assign data_o = data_out;

endmodule

```

- **Simple_Single_CPU Module**

- **Description**

Top Module, 根據Architecture將各模組的線聯起來即可。

Implementation results

- test_data1_result

```

VSIM 10> run -all
# r0 = 0, r1 = 21, r2 = 9, r3 = 1,
# r4 = 20, r5 = 1, r6 = 0, r7 = 0,
# r8 = 0, r9 = 0, r10 = 0, r11 = 0
# ** Note: $stop : C:/Users/justinyeh1995/Desktop/Computer Organization Lab3/testbench.v(32)
# Time: 1010 ns Iteration: 0 Instance: /testbench
# Break in Module testbench at C:/Users/justinyeh1995/Desktop/Computer Organization Lab3/testbench.v line 32
VSIM 11>]

```

- test_data2_result

```

VSIM 8> run -all
# r0 = 0, r1 = 0, r2 = 0, r3 = 0,
# r4 = 0, r5 = 0, r6 = 2, r7 = 5,
# r8 = 7, r9 = 9, r10 = 0, r11 = 0
# ** Note: $stop : C:/Users/justinyeh1995/Desktop/Computer Organization Lab3/testbench.v(32)
# Time: 1010 ns Iteration: 0 Instance: /testbench
# Break in Module testbench at C:/Users/justinyeh1995/Desktop/Computer Organization Lab3/testbench.v line 32
VSIM 9>]

```

- test_data3_result

```

VSIM 6> run -all
# r0 = 0, r1 = 0, r2 = 0, r3 = 0,
# r4 = 0, r5 = 0, r6 = 0, r7 = 0,
# r8 = 0, r9 = 0, r10 = 2, r11 = 2
# ** Note: $stop : C:/Users/justinyeh1995/Desktop/Computer Organization Lab3/testbench.v(32)
# Time: 1010 ns Iteration: 0 Instance: /testbench
# Break in Module testbench at C:/Users/justinyeh1995/Desktop/Computer Organization Lab3/testbench.v line 32
VSIM 7>]

```

Problems encountered and solutions

▼ 在alu.v中，原本將 zero 指定為 `zero <= result == 0?:1:0`，但在思考過後發現，zero 跟 result 同時執行，zero 很有可能因此永遠是32'b0，只是這次測資剛好不會影響到計算結果而已。解法為目前的寫法，用 assign 的方式，讓 result 算完能夠改變 zeroWire 進而改變 zero 使得最終的結果與我們預期的一致，或直接改成src1 與 src2 判斷比較，如此一來可讓 zero 的結果不用依賴result，去除這個問題。

Comment

▼ Decoder matching 經過耗時的比對與修正才讓結果正確。而ALU_Control 的做法了解到老師上課說的從opcode到ALUOp到ALU Control的過程究竟是甚麼意思。是兩件這次學到最多的事情。原本讀這段時一直不確定opcode是怎麼產生ALUOp的，也不知道instruction[30|14:12]的用意，這次一個一個比對才找到其中的關連。寫完作業有更深一層的理解上課內容。